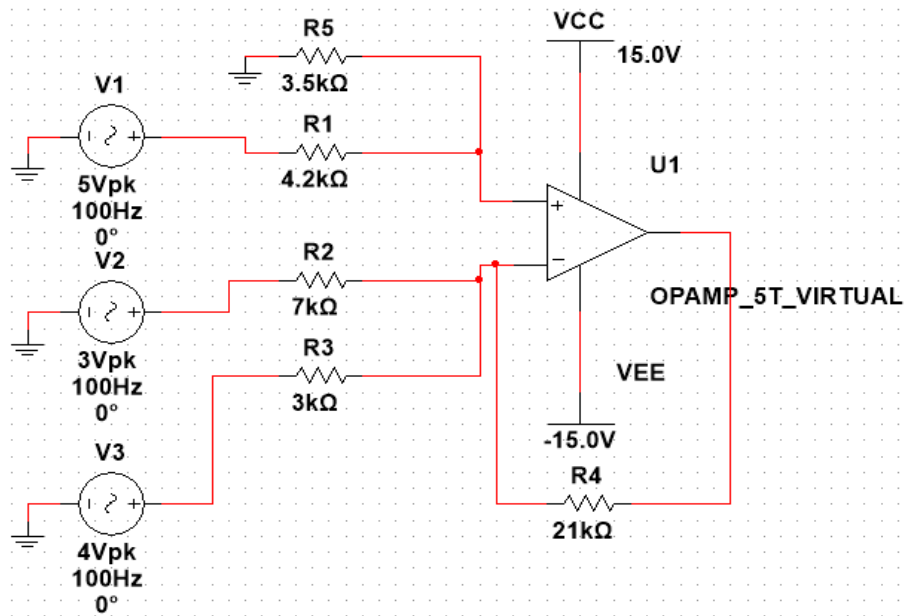


1.

a)




Shivanshu Sahoo

b) Gain of Inverting Amplifier with source resistance R_1 and feedback resistance R_f is $-R_f/R_i$.

Gain of Non-Inverting Amplifier with source resistance R_1 and feedback resistance R_f is $1+(R_f/R_i)$.

c)

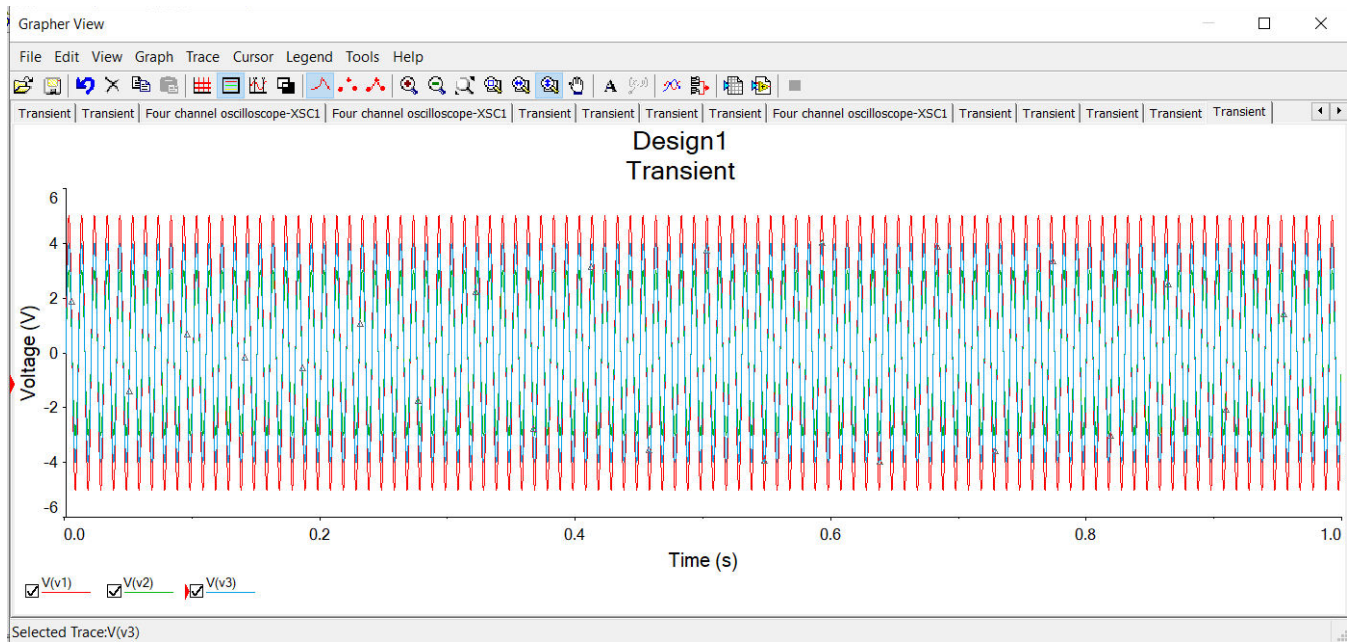

d) The designed circuit is Differential Summer Amplifier.

e)

