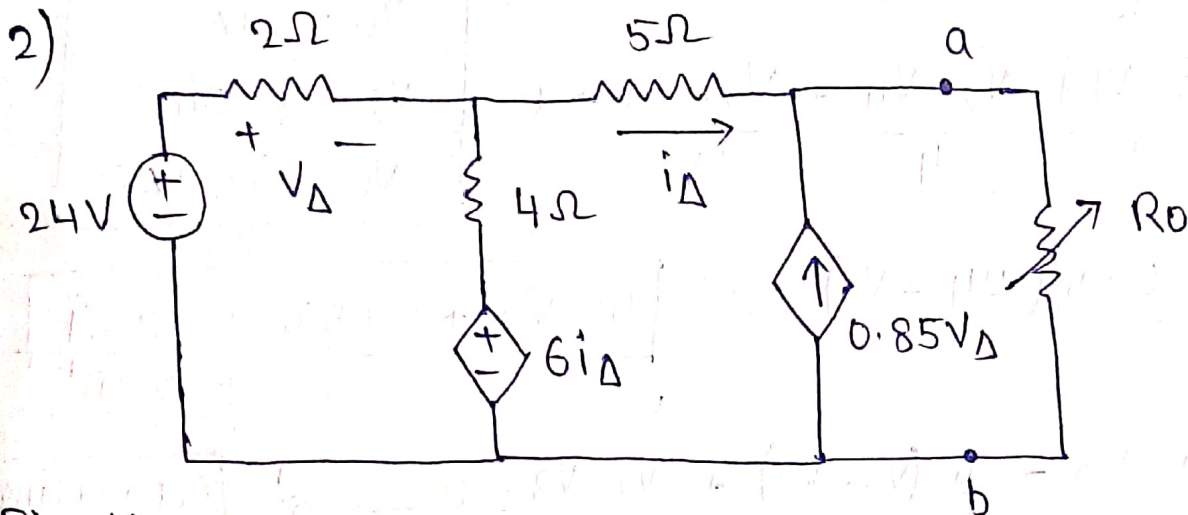


# Network Theory

A. Sai NagaManu


19EE01065

## Home-work-2



Finding the thevenin's equivalent between the terminals a & b:

V<sub>oc</sub>:

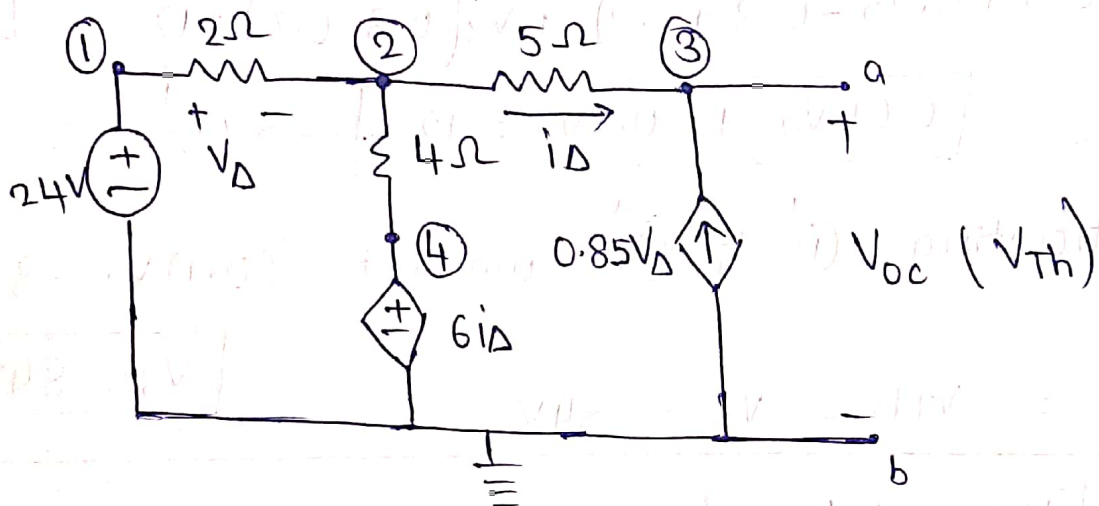

At node-3 :

$$\frac{V_3 - V_2}{5} + (-0.85V_\Delta) = 0 \quad \text{--- ①}$$

At node-2 :

$$\frac{V_2 - V_1}{2} + \frac{V_2 - V_4}{4} + \frac{V_2 - V_3}{5} = 0 \quad \text{--- ②}$$

Extra information:

$$V_4 - 6i_\Delta = 0 \Rightarrow \boxed{V_4 = 6i_\Delta} \quad \text{--- ③}$$

$$V_1 - 24 = 0 \Rightarrow \boxed{V_1 = 24} \quad \text{--- ④}$$

$$\boxed{\begin{array}{l} V_2 - V_3 = 5i_\Delta, \\ V_1 - V_2 = V_\Delta \end{array}} \quad \begin{array}{l} \text{--- ⑤} \\ \text{--- ⑥} \end{array}$$

6- eq's & 6 unknowns. ( $V_1, V_2, V_3, V_4, i_\Delta, V_\Delta$ )

$$1) \Rightarrow \frac{V_3 - V_2}{5} = 0.85 V_\Delta$$

$$2) \Rightarrow \frac{V_2 - V_1}{2} + \frac{V_2 - V_4}{4} + \frac{V_2 - V_3}{5} = 0$$

$$\begin{aligned} V_1 &= 24 \\ V_4 &= 6i_\Delta \\ V_2 - V_3 &= 5i_\Delta \\ V_1 - V_2 &= V_\Delta \end{aligned}$$

$$\frac{V_3 - V_2}{5} = 0.85(24 - V_2) \Rightarrow 0.2V_3 + 0.65V_2 = 20.4 \rightarrow \textcircled{1}'$$

$$\frac{V_2 - 24}{2} + \frac{V_2 - \frac{6}{5}(V_2 - V_3)}{4} + \frac{V_2 - V_3}{5} = 0 \rightarrow \textcircled{2}'$$

converting everything in terms of  $V_2$  &  $V_3$

$$V_2(0.5 + 0.25 - 0.3 + 0.2) + V_3(0.3 - 0.2) = 12$$


$$0.65V_2 + 0.1V_3 = 12 \rightarrow \textcircled{2}'$$

Subtracting  $\textcircled{1}'$  &  $\textcircled{2}'$  we get  $(0.1)V_3 = 8.4$

$$V_3 = 84V$$


$$V_{oc} = V_{Th} = V_3 = 84V$$

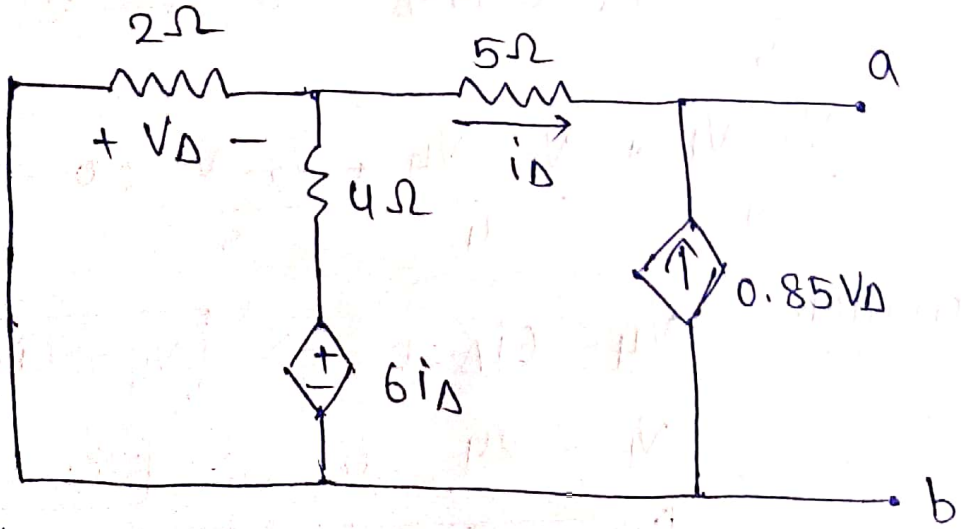Finding  $R_{Th}$ : (short-circuiting the 24V source)



(No independent source is present)

Connecting a test - Source of 1A:

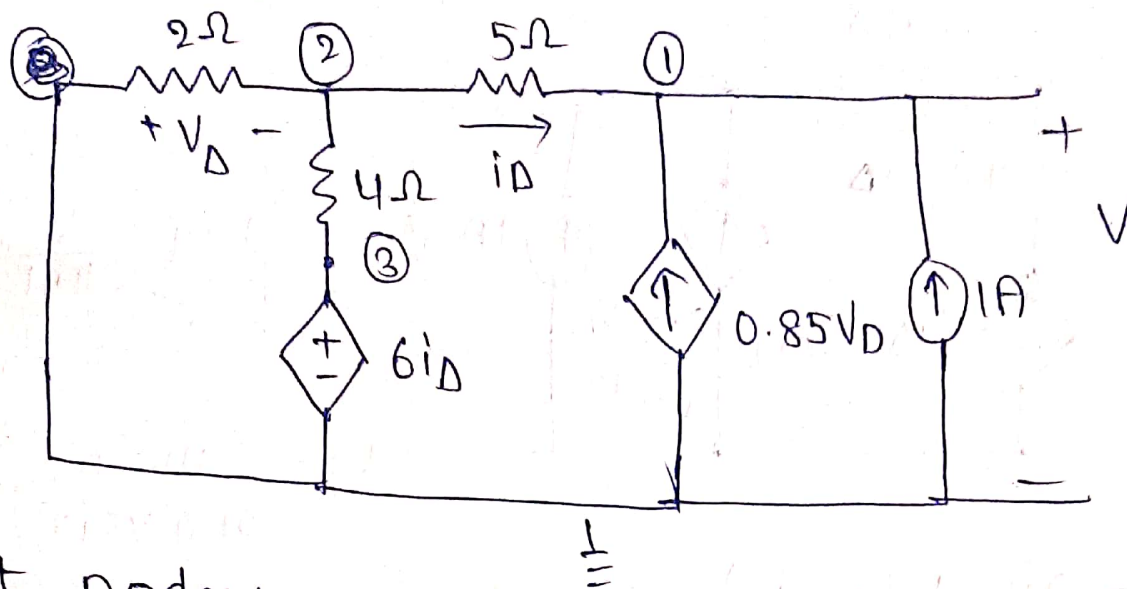

at node-1:  $i_\Delta + 0.85V_\Delta + 1 = 0$

at node-2:  $i_\Delta + \frac{V_2 - V_3}{4} + \frac{V_2}{2} = 0$  — eq (2)

extra information  $V_3 = 6i_\Delta$ ,  $V_2 = -V_\Delta$

converting eq (2) we get,

$$i_\Delta + \frac{-V_\Delta - 6i_\Delta}{4} - \frac{V_\Delta}{2} = 0$$

$$i_\Delta - 0.75V_\Delta - 1.5i_\Delta = 0 \Rightarrow 0.75V_\Delta = -0.5i_\Delta$$

$$i_\Delta = (V_\Delta)(-1.5)$$

we get  $i_\Delta + 0.85V_\Delta + 1 = 0 \Rightarrow -1.5V_\Delta + 0.85V_\Delta + 1 = 0$


$$V_\Delta = \frac{1}{1.5 - 0.85} = 1.538 \text{ V}$$

$$V_1 = V_2 - 5i_\Delta = -V_\Delta + 7.5V_\Delta = 6.5V_\Delta = 10 \text{ V}$$

$$R_{Th} = \frac{V_1}{1 \text{ A}} = 10 \Omega$$




Our modified circuit is

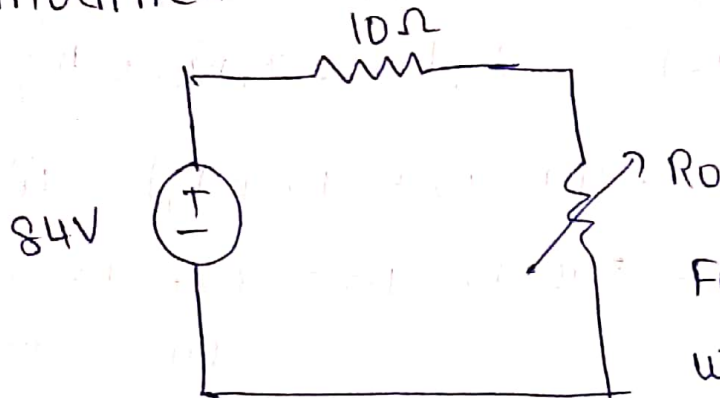


For  $R_o = R_{Th} = 10\Omega$   
we will get  
max power

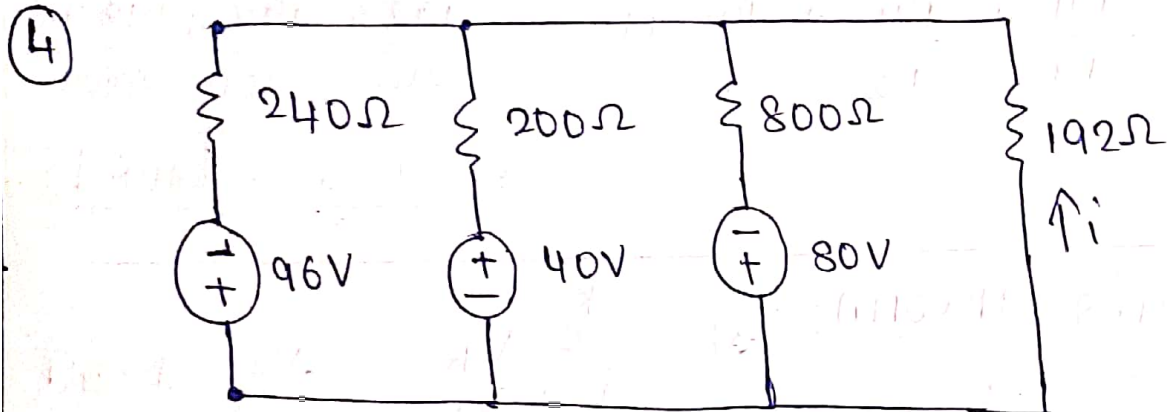
$$\text{max power} = \frac{V_{Th}^2}{4 R_{Th}} = \frac{84 \times 84}{4 \times 10} = \boxed{176.4 \text{ W}}$$



a) By source transformation:

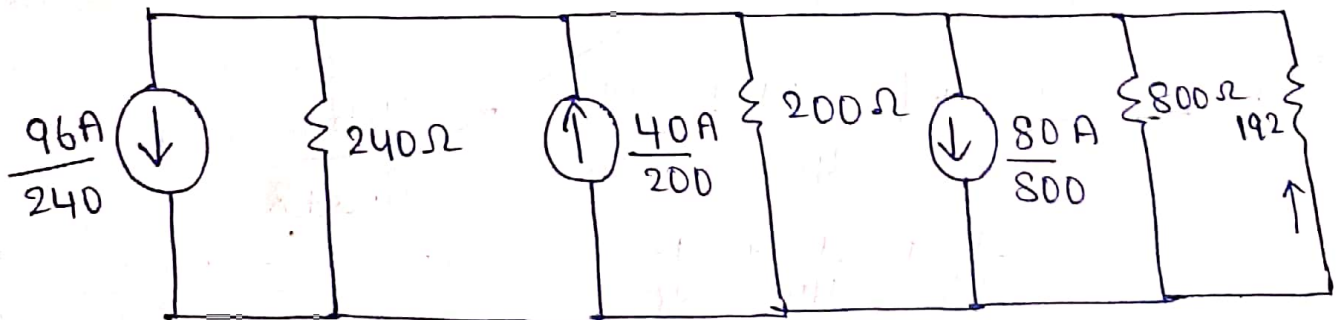

Current Sources can be grouped together!

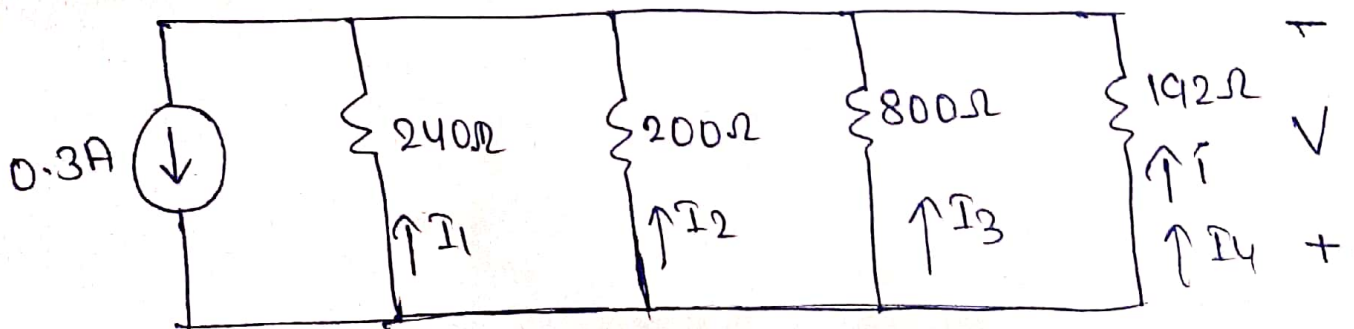


as they are connected in parallel  $V$  is same  
 $I_1 R_1 = I_2 R_2 = I_3 R_3 = I_4 R_4 = V$

By KCL,  $0.3 = (I_1 + I_2 + I_3 + I_4)$  Where  
 $R_1 = 240\Omega$ ,  $R_2 = 200\Omega$ ,  $R_3 = 800\Omega$ ,  
 $R_4 = 192\Omega$

$$0.3 = I_4 \frac{R_4}{R_1} + I_4 \frac{R_4}{R_2} + I_4 \frac{R_4}{R_3} + I_4$$

$$I_4 = i = \frac{0.3}{\frac{R_4}{R_1} + \frac{R_4}{R_2} + \frac{R_4}{R_3} + 1} = \frac{0.3}{\frac{192}{240} + \frac{192}{200} + \frac{192}{800} + 1}$$
$$= \frac{0.3}{3} = \boxed{0.10A}$$

By millman's theorem:

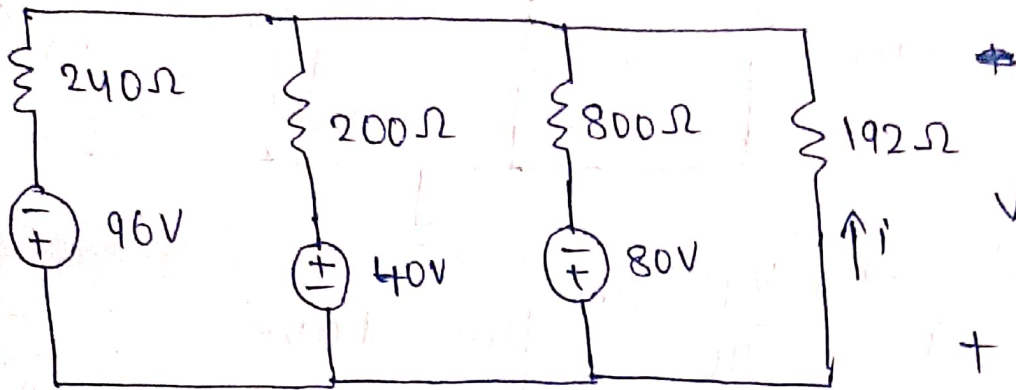

polarity is properly considered)


$$V = \frac{\sum_{i=1}^3 \frac{\epsilon_i}{R_i}}{\sum_{i=1}^3 \frac{1}{R_i}}, \text{ then } i = \frac{V}{192}$$

[considered as '0' voltage source]

$$\Rightarrow V = \frac{\frac{96}{240} - \frac{40}{200} + \frac{80}{800} + \frac{0}{192}}{\frac{1}{240} + \frac{1}{200} + \frac{1}{800} + \frac{1}{192}} = \frac{0.3}{0.015625}$$

$$V = 19.2V \Rightarrow i = \frac{19.2}{192} = 0.1A$$

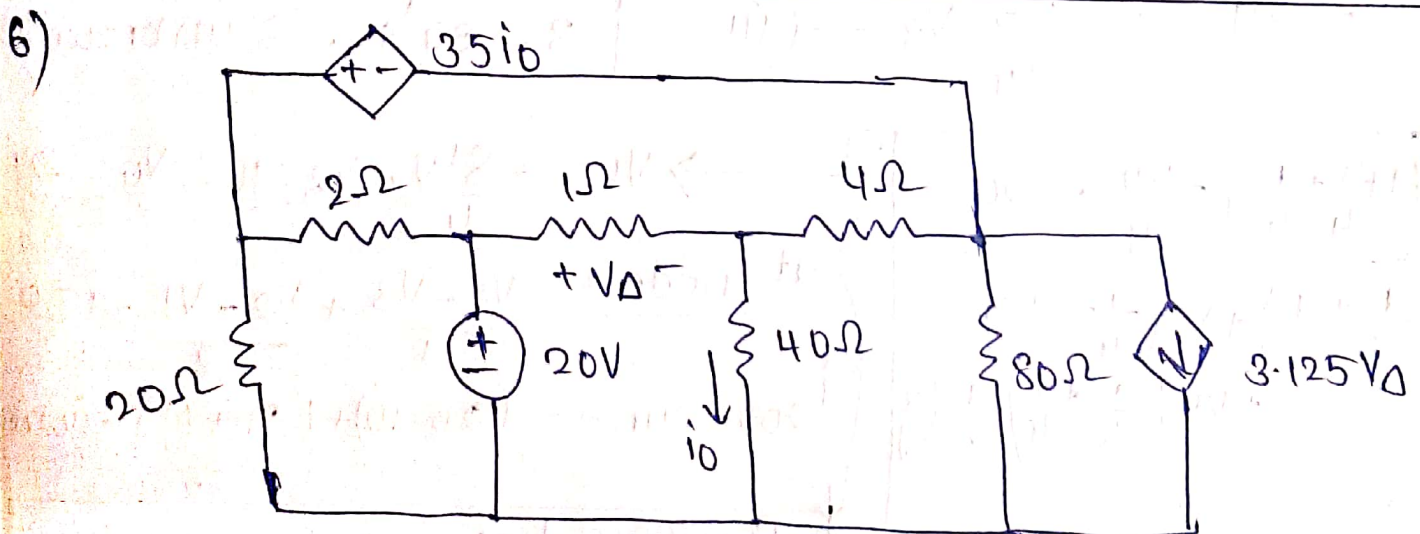
By both source transformation and millman's theorem  $i$  through  $192\Omega$  came out to be 0.1A



Power developed by 20V source = ?



Using nodal analysis:

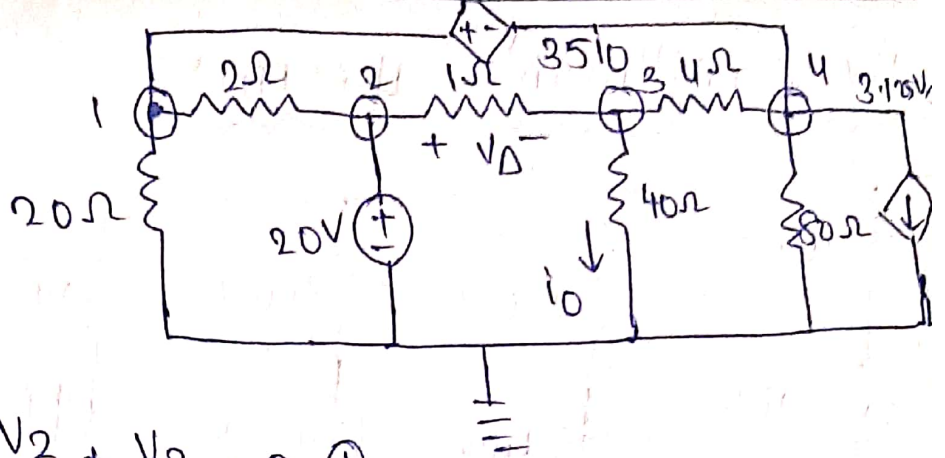

At node 3:

$$\frac{V_3 - V_4}{4} + \frac{V_3 - V_2}{1} + \frac{V_3}{40} = 0 \quad \text{--- (1)}$$

we have

$$V_2 = 20V, \quad i_0 = \frac{V_3}{40}$$

considering (1) & (4) as super node we get

$$\frac{V_1}{20} + \frac{V_1 - V_2}{2} + \frac{V_4}{80} + 3.125V_\Delta + \frac{V_4 - V_3}{4} = 0 \quad \text{--- (2)}$$

$$V_1 - V_4 = 35i_0$$

$$V_1 - V_4 = \frac{35V_3}{40} \quad \text{--- (3)}$$

$$V_\Delta = V_2 - V_3 = 20 - V_3$$

From (1)

$$\frac{V_3 - V_4}{4} + V_3 - 20 + \frac{V_3}{40} = 0 \quad \text{--- (I)}$$

$$\frac{V_1}{20} + \frac{V_1 - 20}{2} + \frac{V_4}{80} + 3.125(20 - V_3) + \frac{V_4 - V_3}{4} = 0 \quad \text{--- (II)}$$

$$V_1 - V_4 = \frac{35}{40} V_3 \quad \text{--- (III)} \quad [3 \text{ eq's, 3 unknowns}]$$

$$V_3 \left( 1 + \frac{1}{4} + \frac{1}{40} \right) - \frac{V_4}{4} = 20$$

$$V_1 \left( \frac{1}{20} + \frac{1}{2} \right) + V_3 \left( -\frac{1}{4} - 3.125 \right) + V_4 \left( \frac{1}{80} + \frac{1}{4} \right) = \frac{10 \times 20}{3.125}$$

$$V_1 - V_4 - \frac{35}{40} V_3 = 0$$

$$\rightarrow V_1 = -\frac{81}{4}V, \quad V_3 = 10V, \quad V_4 = -29$$


$$\text{at node-2} \quad \frac{V_2 - V_3}{1} + \frac{V_2 - V_1}{2} - i = 0$$

$$i_{20V \text{ source}} = (20 - 10) + \left( \frac{20 + \frac{81}{4}}{2} \right) = 30.125A$$

\* Power delivered by 20V source

$$= 20 \times 30.125 = 602.5W$$

8)

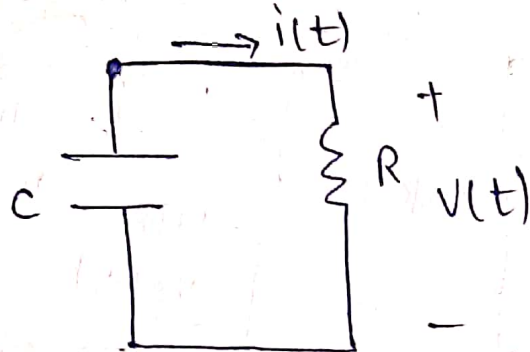

Given  $V(t) = 72e^{-500t} \text{ V}(t \geq 0)$   
 $i(t) = 9e^{-500t} \text{ mA}(t \geq 0)$

Differential equation:  $C \frac{dV}{dt} + \frac{V}{R} = 0$

$$\frac{dV}{dt} = -\frac{V}{RC}$$

$$V = V_0 e^{-t/RC} \quad t \geq 0$$

Comparing with given data, we get  $\tau = RC = \frac{1}{500}$   
 $V_0 = 72 \text{ V}$  &  $RC = \frac{1}{500}$

we can also say that

$$V_C(0^-) = V_C(0^+) = 72 \text{ V}$$

at  $t=0$ ,  $i(0) = 9 \text{ mA}$

$$V(0) = V_0 = 72 \text{ V}$$

$$V(0) = i(0) R$$

$$72 = 9 \times 10^{-3} R \Rightarrow R = 8 \text{ k}\Omega$$

$\therefore$  Just after  $C$  is connected to  $R$  it behaves as a dc source and then decays exponentially


✓ we also have  $RC = \frac{1}{500} \Rightarrow C = \frac{1}{500 \times 8 \times 10^3}$   
 (time constant =  $1/500$ )  
 $C = 250 \text{ nF}$

✓ Initial energy stored in the capacitor


$$= \frac{1}{2} C V_0^2 = \frac{1}{2} \times 250 \times 10^{-9} \times 72 \times 72$$
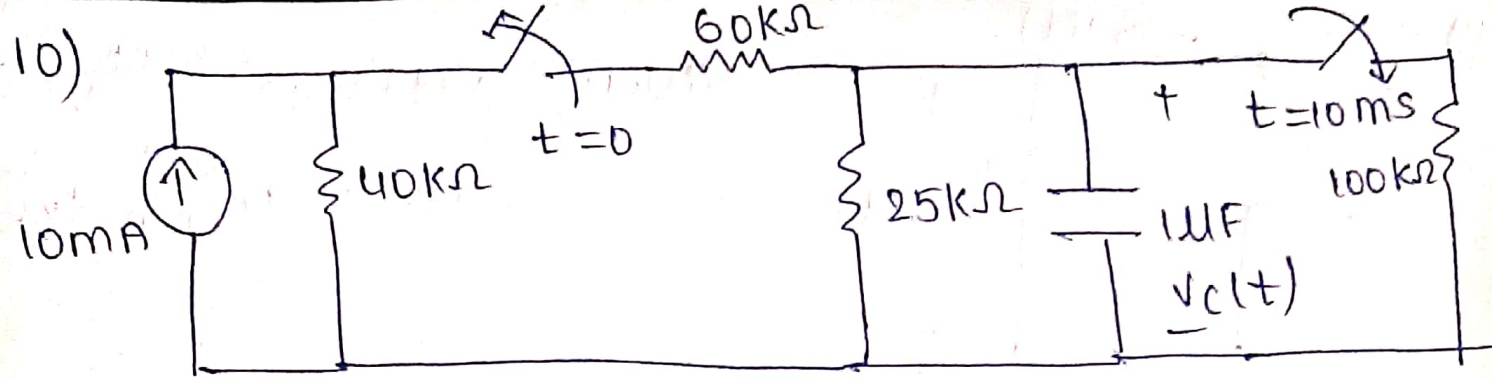
$$= 648 \times 10^{-6} \text{ J} \quad (648 \text{ }\mu\text{J})$$





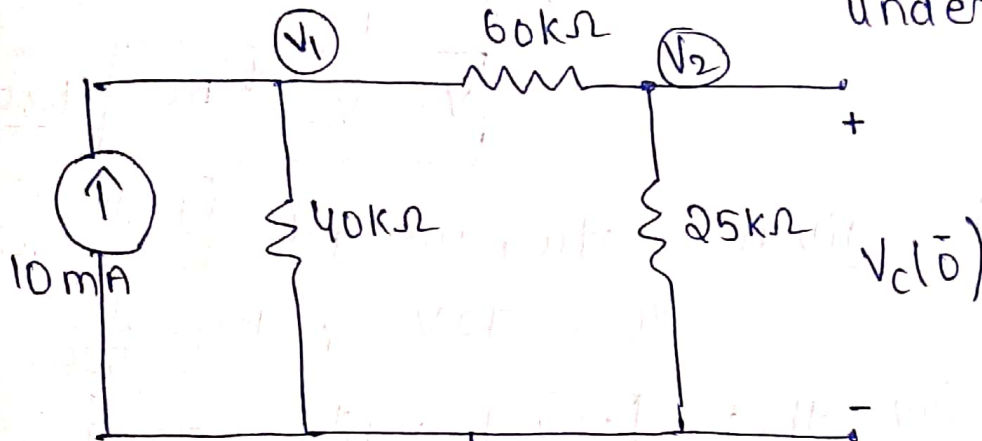For  $t \leq 0$ : (1μF capacitor will be considered as open circuit as it is under dc source for long time)



node-1

$$\frac{V_1}{40} + \frac{V_1 - V_2}{60} - 10 = 0$$

node-2

$$\frac{V_2}{25} + \frac{V_2 - V_1}{60} = 0 \Rightarrow V_2 \left( \frac{1}{25} + \frac{1}{60} \right) = \frac{V_1}{60}$$

$$V_2 \left( 1 + \frac{60}{25} \right) = V_1$$

$$\boxed{V_1 = V_2 \frac{17}{5}}$$

$$V_1 \left( \frac{1}{40} + \frac{1}{60} \right) - \frac{V_2}{60} = 10$$

$$\frac{17V_2}{5} \left( \frac{3+2}{120} \right) - \frac{V_2}{60} = 10$$



$$\frac{17V_2}{120} - \frac{2V_2}{120} = 10$$

$$\frac{15V_2}{120} = 10$$

$$\boxed{V_2 = 80V}$$

$$\Rightarrow \boxed{V_c(0^-) = 80V}$$

For  $0 \leq t \leq 10 \text{ ms}$

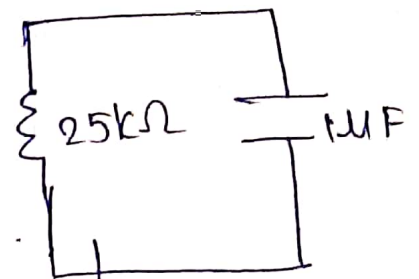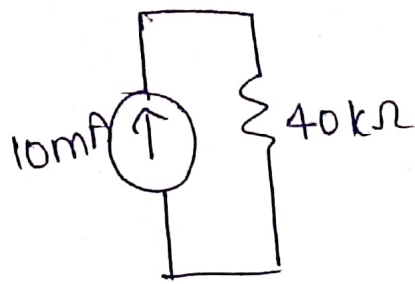


$$V_C = V_0 e^{-t/RC}$$

$$V_0 = V_C(0^+) = V_C(0^-) = 80$$

$$RC = 25 \times 10^3 \times 10^{-6} = 25 \times 10^{-3} \Rightarrow V_C(t) = 80 e^{-\frac{t \times 10^3}{25}}$$

$$\boxed{V_C(t) = 80 e^{-40t} \text{ V}}$$

For  $t \geq 10 \text{ ms}$

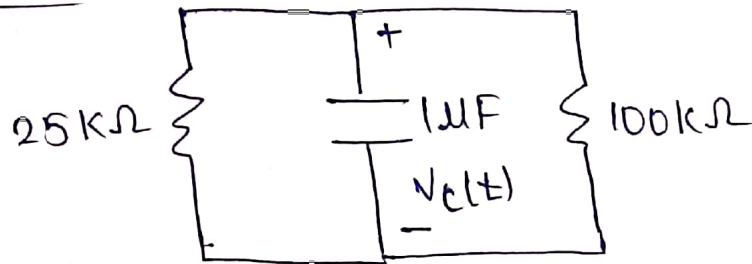

$$R_{eq} = \frac{25 \times 100}{125} = 20 \text{ k}\Omega$$

$$\tau = RC = 20 \times 10^3 \times 10^{-6} = \boxed{20 \times 10^{-3}}$$

$$C = 1 \mu\text{F}$$

$$V_C(10 \text{ ms}^+) = V_C(10 \text{ ms}^-) = 80 \times e^{-40 \times 10 \times 10^{-3}}$$

$$\boxed{V_C(10^-) = 53.62 \text{ V}}$$

For  $t \geq 10 \text{ ms}$

$$V_C(t) = 53.62 e^{-\frac{(t - 10 \times 10^{-3})}{20} \times 10^3}$$

$$= 53.62 e^{-50(t - 0.01)} \text{ V}$$

$$V_C(t) = \begin{cases} 80 & t \leq 0 \\ 80 e^{-40t} & 0 \leq t \leq 10 \text{ ms} \\ 53.62 e^{-50(t - 0.01)} & 10 \leq t < \infty \text{ ms} \end{cases}$$