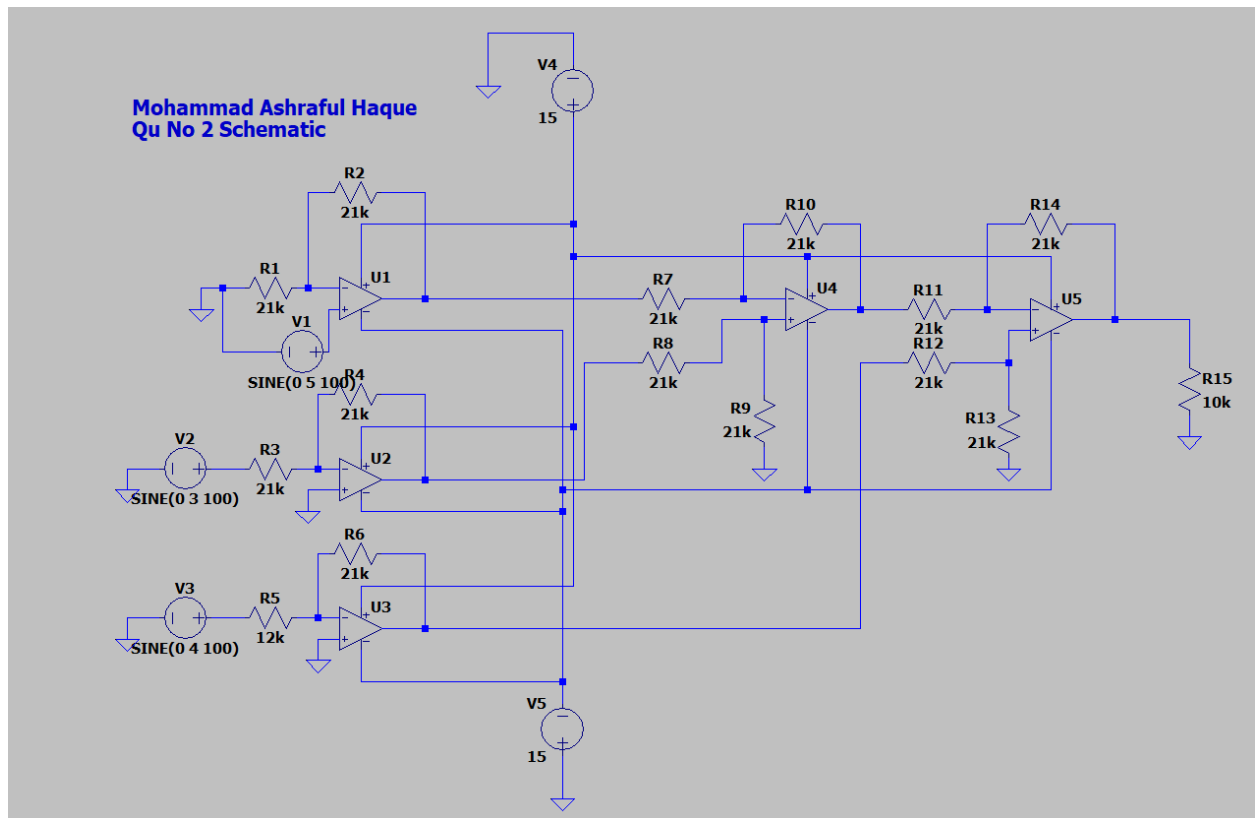


a)



Ans to the qu no- 02

b)

Inverting amplifier close loop gain,

$$A_v = - \frac{R_f}{R_i}$$

Non Inverting amplifier close loop gain,

$$A_v = 1 + \frac{R_f}{R_i}$$

d) The circuit designed have three types of amplifiers:

- ① Non-inverting amplifier
- ② Inverting amplifier
- ③ Difference amplifier