

Ans to the qu no-04

d) Capacitor behaves as open-circuit in DC analysis after it is fully charged.