

ANALOG CIRCUIT DESIGN


WISSENAIRE

Simulation Report *And Solutions*

Name	-	Rhea Singh
Wissenaire's ID	-	W21R10531
Department	-	Electrical Engineering
Date of Submission	-	2 April , 2021

Solution No. 3

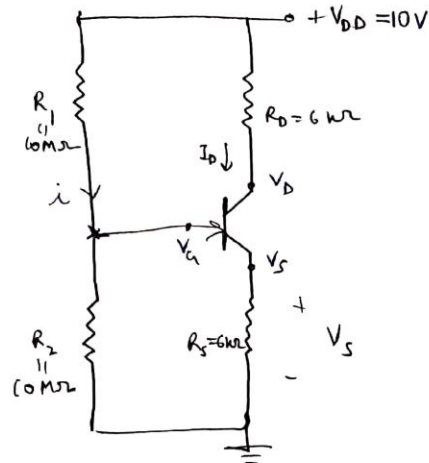a) Solved the given circuit theoretically,



$$V_t = 1V \quad \mu_n C_{ox} \left(\frac{W}{L} \right) = 1 \text{ mA/V}^2$$

In MOSFET, no current going in gate.

$$i = \frac{10}{10\text{M}\Omega + 10\text{M}\Omega} = 0.5 \mu\text{A}$$

$$V_G = V_{TH} = \frac{10}{2} = 5V$$

$$\Rightarrow V_G = 5V$$

$$V_D = 10 - I_D (6k\Omega)$$

$$V_S = 0 + I_D (6k\Omega)$$

assuming transistor to be in saturation,

$$V_{GS} = 5 - I_D (6k\Omega)$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$= \frac{1}{2} \times 1 \text{ mA/V}^2 \times (4 - 6I_D)^2$$

$$\therefore I_D = 0.88 \text{ mA and } 0.5 \text{ mA}$$

also verify,

$$V_S = 5.28 \text{ when } I_D = 0.88 \text{ mA}$$

$$V_{GS} = -0.28$$

$$\Rightarrow V_{GS} < V_t \text{ Cutoff}$$

X wrong assumption

so $I_D = 0.88 \text{ mA}$ not possible.

Now, $I_D = 0.5 \text{ mA}$

$$\boxed{V_S = 3V}$$

$$\boxed{V_D = 7V}$$

$$V_{DS} = 4V \quad V_{GS} = 2V$$


&

$$V_{DS} > V_{GS} - V_t$$

✓ correct assumption.

$$\therefore \boxed{I_D = 0.5 \text{ mA}}$$

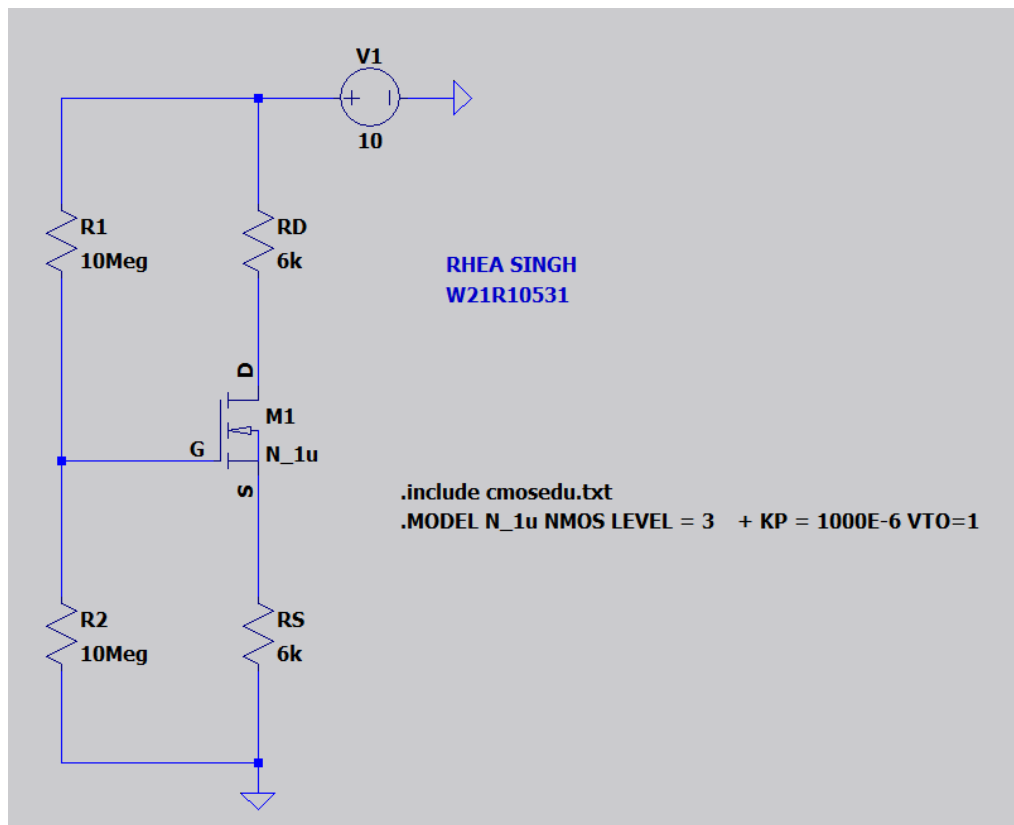b) The screenshot of schematic consisting designed circuit :



c) The screenshot of voltages and currents obtained by performing DC Op simulation :

* C:\Users\rhea8\OneDrive\Desktop\Analog_Circuit_Design\Draft5.asc

--- Operating Point ---		
V(d) :	7	voltage
V(g) :	5	voltage
V(s) :	3	voltage
V(n002) :	3.15305	voltage
V(n001) :	10	voltage
Id(M1) :	0.0005	device_current
Ig(M1) :	0	device_current
Ib(M1) :	1.9871e-016	device_current
Is(M1) :	-0.0005	device_current
I(Rd) :	0.0005	device_current
I(Rs) :	0.0005	device_current
I(R2) :	5e-007	device_current
I(R1) :	5e-007	device_current
I(V1) :	-0.0005005	device_current

- d) The current through gate of MOSFET is zero because it is insulated with the oxide layer so the current cannot pass through it.
- e) The bias employed for the given circuit is that the transistor is in saturation.
- f) The significance of threshold voltage in MOSFET is that as threshold voltage is the minimum gate-to-source voltage $V_{GS(th)}$ that is needed to create a conducting path between the source and drain terminals so it is an important scaling factor to maintain power efficiency.