

ANALOG CIRCUIT DESIGN

WISSENAIRE


Simulation Report *And Solutions*

Name	-	Rhea Singh
Wissenaire's ID	-	W21R10531
Department	-	Electrical Engineering
Date of Submission	-	2 April , 2021

Solution No. 4

a)

DC Analysis

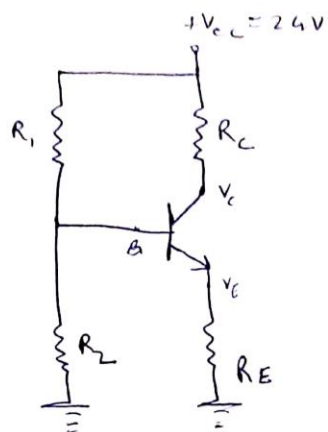

$$A_V(AC) = -100$$

$$I_C = 4 \text{ mA}$$

$$V_{CE} = 12 \text{ V}$$

$$I_{C(sat)} = 8 \text{ mA}$$

$$\text{DC current gain } (\beta) = 100$$

$$R_2 \leq \frac{(\beta R_E)}{10}$$

$$V_{BE} = 0.7 \text{ V}$$

$$V_C = 24 - I_C R_C$$

$$V_E = -I_C R_E$$

$$V_{CE} = 12 \text{ V}$$

$$24 - 8 \text{ mA } R_C - 8 \text{ mA } R_E = 12$$

$$12 = 8 \text{ mA } (R_C + R_E)$$

$$\frac{3 \text{ k}\Omega}{2} = R_C + R_E$$

$$\frac{3 \text{ k}\Omega}{2} = 101 R_E$$

$$R_E = \frac{3 \text{ k}\Omega}{202} = 14.85 \text{ }\Omega$$

$$R_E = 14.85 \text{ }\Omega$$

$$R_E = \frac{0.0297 \text{ k}\Omega}{2} \approx 0.015 \text{ k}\Omega$$

$$R_C = \frac{2.97 \text{ k}\Omega}{2} \approx 1.5 \text{ k}\Omega$$

$$R_{Th} = 0.1(\beta + 1) R_E \quad \text{so from } R_{Th} \text{ we can get } R_1, R_2 \text{ also}$$

d) In DC operation, the capacitors behave as open circuit because the ω is 0 for DC and the impedance of capacitance is $1/\omega C$.

e) The specification given as $R_2 \leq (\beta R_E)/10$ is to ensure bias stability.

g) The frequency response of a CE amplifier and explain why does it look like that is because in the CE amplifier it depends on the frequency of the ac source.