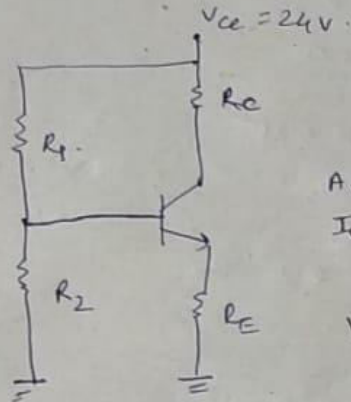


4.

a)

4. (a)



$$A_v(oc) = 100$$

$$I_C = 4 \text{ mA}$$

$$\beta = 100$$

$$V_{CE} = 12 \text{ V}$$

Here we have to take value of R_2 such that

$$R_2 \leq \frac{\beta R_E}{10}$$

Hence for this condition $I_B = 0$.

$$\text{hence } I_C = I_E$$

using KVL

we have

$$\Rightarrow V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$\Rightarrow 24 - I_C R_C - 12 - I_E R_E = 0$$

$$\Rightarrow 12 = I_C (R_C + R_E)$$

$$\Rightarrow \frac{12}{4 \text{ mA}} = R_C + R_E$$

$$\Rightarrow R_C + R_E = 3 \text{ k}\Omega$$

$$A_v(oc) = -100 = -\frac{R_C}{r_e}$$

$$r_e \approx \frac{V_T}{I_C} = \frac{V_T}{I_E} = \frac{25 \text{ mV}}{4 \text{ mA}} = \frac{25}{4} \Omega$$

$$R_C = \frac{25}{4} \times 100$$

$$= 625 \Omega$$

$$R_E = 3000 - 625$$

$$= 2375 \Omega$$

$$\Rightarrow \frac{24}{R_1 + R_2} \times R_2 = 0.7 = I_E \times 4 \text{ mA}$$

$$\Rightarrow \frac{R_2}{R_1 + R_2} = \frac{7}{40}$$

Now taking $R_2 = \frac{\beta R_E}{10}$


$$= \frac{100 \times 2375}{10}$$

$$= 23750 \Omega$$


$$= 23.75 \text{ k}\Omega$$

$$R_1 = \frac{33 \times 23.75 \text{ k}}{7} = 111.965 \text{ k}\Omega$$

b)

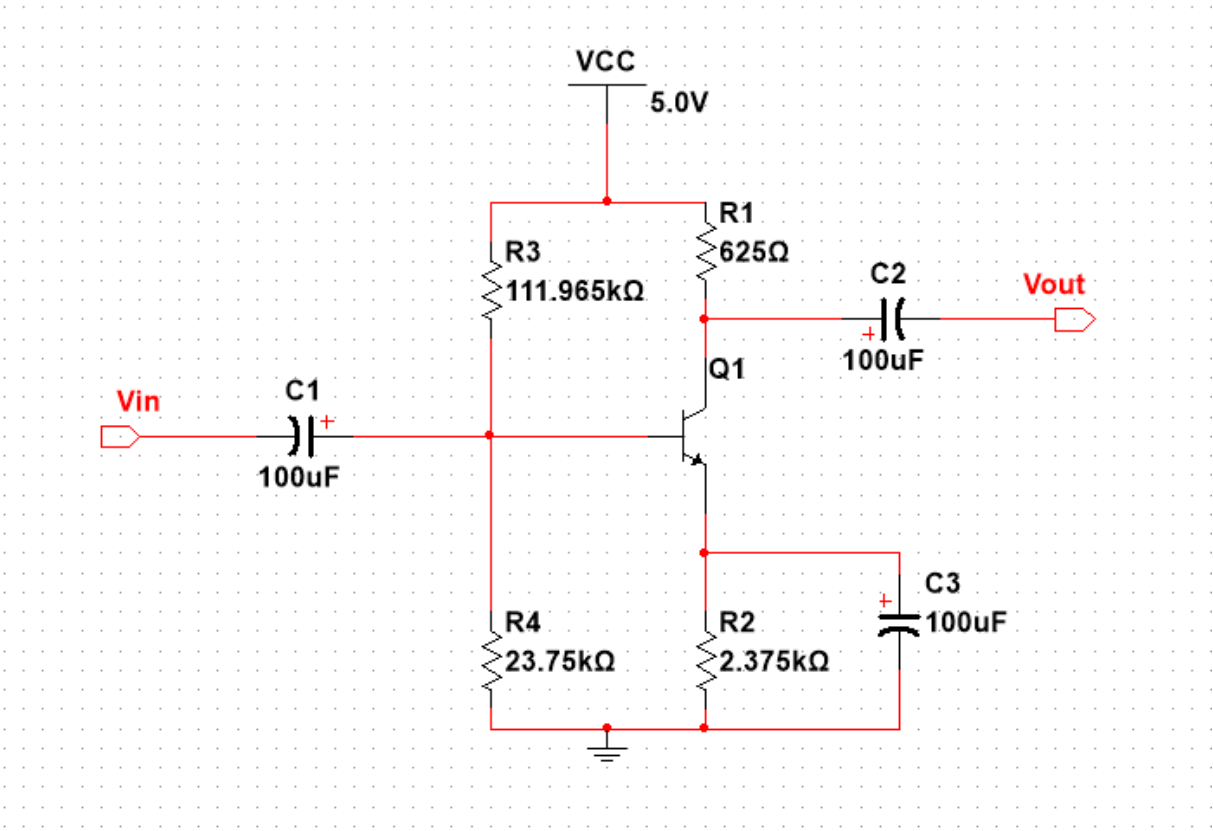

c)

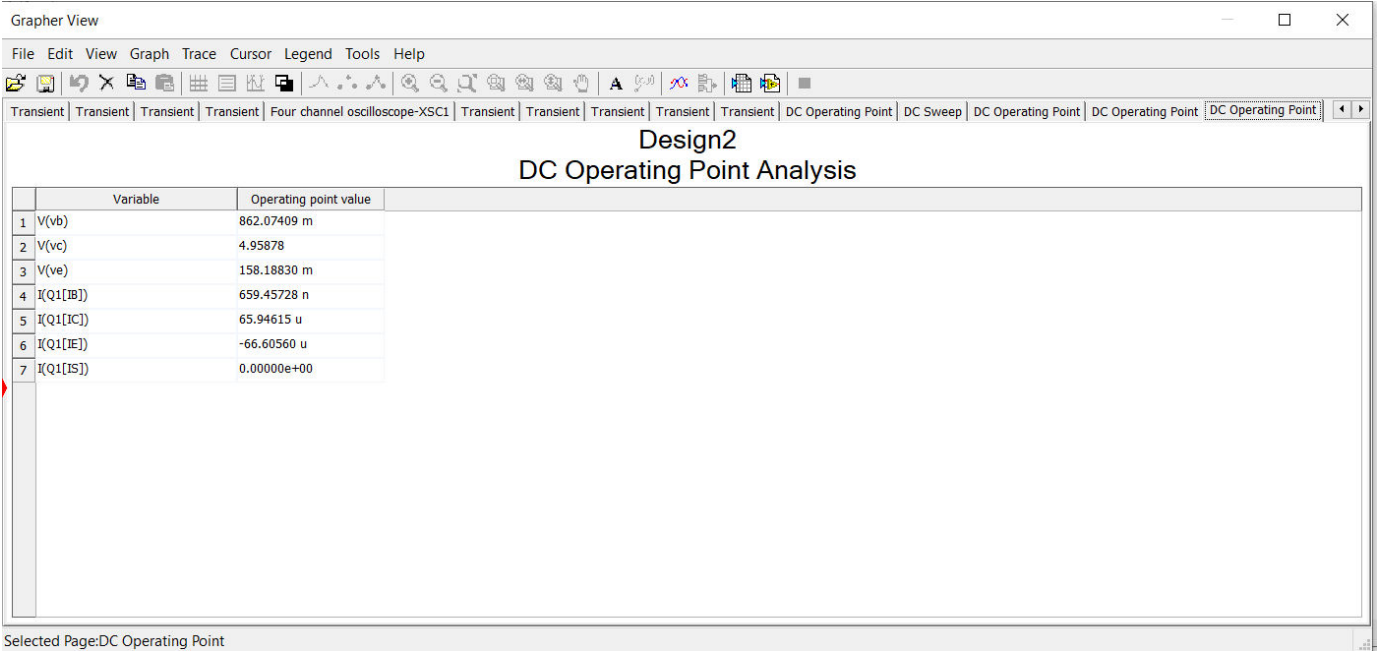

d)

(d) In DC operation the capacitors are open circuited because we know the frequency of supply in DC is zero

$$X_C = \frac{1}{j\omega C} \quad \text{so } X_C = \infty$$

Here it is replaced with an open circuit.

e)

(e) The resistance R_i is the equivalent resistance between base and ground for the transistor with an emitter resistor R_E that the reflected resistance between base and emitter is defined by $R_i = (\beta + 1) R_E$.

If R_i is much larger than the resistance R_2 , the current I_B will be much smaller than I_2 so

I_B is essentially ≈ 0 .

so $R_i \approx \beta R_E$ the approximation can be done.


$$\beta R_E \geq 10 R_2$$

f)

(f)

since from the above result
EB Junction is +ve hence
forward bias and V_{CB} is
-ve so reverse bias hence
it operate in active region.

g)

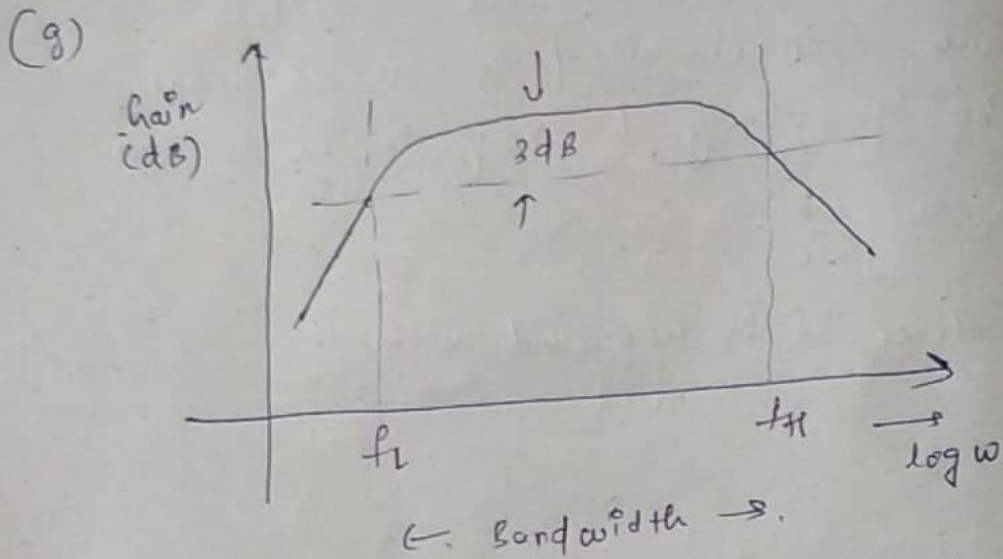

Low frequency.

- At low frequency the gain reduces because of coupling capacitor which causes voltage drop.
- Bypass capacitor which didn't completely bypass the source resistance or ammeter resistance causing -ve feedback.

High frequency

- It was due to internal or parasitic capacitances. Now in ~~BJT~~ BJT these capacitors include the capacitance between gate and source.